

Please write clearly in block capitals.

Centre number

--	--	--	--	--

Candidate number

--	--	--	--

Surname

---

Forename(s)

---

Candidate signature

---

I declare this is my own work.

# A-level PHYSICS

## Paper 3 Section B Electronics

### Materials

For this paper you must have:

- a pencil and a ruler
- a scientific calculator
- a Data and Formulae Booklet
- a protractor.

### Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer **all** questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- If you need extra space for your answer(s), use the lined pages at the end of this book. Write the question number against your answer(s).
- Do all rough work in this book. Cross through any work you do not want to be marked.
- Show all your working.

### Information

- The marks for questions are shown in brackets.
- The maximum mark for this paper is 35.
- You are expected to use a scientific calculator where appropriate.
- A Data and Formulae Booklet is provided as a loose insert.

Time allowed: The total time for both sections of this paper is 2 hours. You are advised to spend approximately 50 minutes on this section.

For Examiner's Use	
Question	Mark
1	
2	
3	
4	
5	
<b>TOTAL</b>	



**There are no questions printed on this page**

*Do not write  
outside the  
box*

**DO NOT WRITE ON THIS PAGE  
ANSWER IN THE SPACES PROVIDED**




## Section B

Answer **all** questions in this section.

0 1

**Figure 1** shows a circuit containing an ideal operational amplifier. A signal  $V_{in}$  is applied to one of the amplifier inputs.

Figure 1

 

0 1 . 1

Draw an **X** on the circuit in **Figure 1** to indicate a virtual earth point.

[1 mark]

0 1 . 2

Show that the closed loop voltage gain for the amplifier in **Figure 1** is given by:

$$\frac{R_f}{R_{in}} = - \frac{V_{out}}{V_{in}}$$

State any assumptions made in your answer.

[2 marks]

assumptions \_\_\_\_\_

\_\_\_\_\_


Question 1 continues on the next page

Turn over ►




**0 1 . 3** Figure 2A shows the input signal  $V_{in}$  that is applied to the circuit in Figure 1.

**Figure 2A**

 

**Figure 2B**

 

The circuit in **Figure 1** has a closed loop gain of  $-20$  and has power-supply voltages of  $\pm 6.0$  V.

Draw, on **Figure 2B**, the output waveform from the operational amplifier circuit over the same time interval as that shown on **Figure 2A**.

**[2 marks]**



0 1 . 4


A student converts the circuit in **Figure 1** into one that will add two input signals  $V_1$  and  $V_2$ .

The new circuit produces an output voltage  $V_{\text{out}}$  so that:

$$V_{\text{out}} = -(1.5V_1 + 0.75V_2)$$

The circuit is to include a  $27 \text{ k}\Omega$  feedback resistor.

Complete **Figure 3** to show the circuit that the student constructs.  
Annotate your circuit with the values of any additional components.

 **[3 marks]****Figure 3**

Turn over for the next question


Turn over ►



0 2

**Figure 4** shows a logic system made of logic gates labelled 1 to 6. The logic system has inputs **A** and **B** and outputs **X**, **Y** and **Z**.

Figure 4

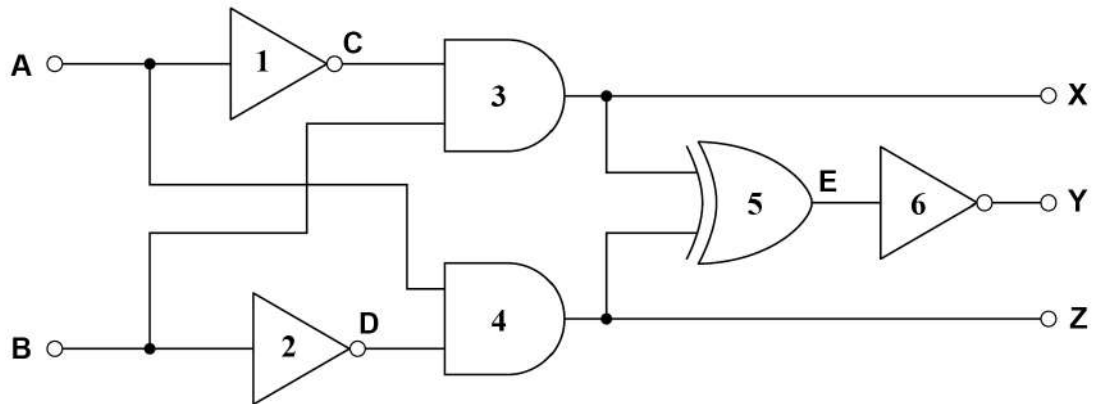

0 2

. 1

Write the simplest Boolean algebra expression for output **X** in terms of inputs **A** and **B**.

[2 marks]

**X** = \_\_\_\_\_

0 2

. 2

State the name of logic gate **5** in **Figure 4**.

[1 mark]

\_\_\_\_\_

0 2

. 3

Complete **Table 1**, the truth table for this logic system.

[2 marks]

Table 1

B	A	C	D	E	X	Y	Z
0	0	1	1	0			
0	1	0	1	1			
1	0	1	0	1			
1	1	0	0	0			



- 0 2 . 4** Suggest a single logic gate that can replace the combination of gates **5** and **6** in this system.

[1 mark]

- 0 2 . 5** The logic system in **Figure 4** is designed to indicate which of inputs **A** and **B** has the larger binary value, or whether the values are the same. Each decision is indicated by one of the outputs **X**, **Y** or **Z** becoming a logic 1

Which row identifies the outputs **X**, **Y** and **Z**?  
Tick (✓) **one** box.

[1 mark]

<b>X</b>	<b>Y</b>	<b>Z</b>	
<b>A = B</b>	<b>A &lt; B</b>	<b>A &gt; B</b>	<input type="checkbox"/>
<b>A &lt; B</b>	<b>A = B</b>	<b>A &gt; B</b>	<input type="checkbox"/>
<b>A &lt; B</b>	<b>A &gt; B</b>	<b>A = B</b>	<input type="checkbox"/>
<b>A &gt; B</b>	<b>A = B</b>	<b>A &lt; B</b>	<input type="checkbox"/>

7
---

**Turn over for the next question**

**Turn over ►**




0 3

**Figure 5** shows the output signal from the tuner circuit of a radio receiver.

The radio carrier wave is amplitude modulated by a single-frequency test tone.

**Figure 5**

 

0 3 . 1

Determine the frequency, in kHz, of the carrier wave.

[1 mark]

frequency of carrier wave = \_\_\_\_\_ kHz

0 3 . 2

Determine the frequency, in kHz, of the test tone.

[2 marks]

frequency of test tone = \_\_\_\_\_ kHz





**0 3 . 3** State **one** advantage of using frequency modulation (FM) rather than amplitude modulation (AM).

**[1 mark]**

---



---

**0 3 . 4** The frequency range of the FM radio band in the UK is 88 to 108 MHz.

The FM stations are allocated centre frequencies that start at 88.100 MHz and are separated by 200 kHz.

Calculate the maximum number of stations allowed within the range.

**[1 mark]**

maximum number of stations = \_\_\_\_\_

**0 3 . 5** A radio station broadcasting on FM transmits a maximum audio frequency of 15 kHz and has a frequency deviation of  $\pm 75$  kHz.

Deduce whether the radio station fits the FM bandwidth allocation in the UK.

**[2 marks]**

---



---



---


7

Turn over ►



0 4

**Figure 6** shows a type of NOT gate called a Schmitt Trigger. This is connected to a capacitor of capacitance  $C$  and a resistor of resistance  $R$  to make an oscillator circuit. The circuit is used to produce continuous clock pulses.

 **Figure 6**

$V_{out}$  switches HIGH or LOW when the input voltage  $V_c$  passes through one of two trigger voltage values.

The output voltage  $V_{out}$  switches to:

- LOW when  $V_c$  rises and reaches the upper trigger voltage  $V_U$
- HIGH when  $V_c$  falls and reaches the lower trigger voltage  $V_L$ .



0	4	.	1
---	---	---	---

Initially the capacitor is uncharged and  $V_c$  is at 0 V.

Explain the sequence of actions of this circuit as the output goes through one full cycle. The first two stages have been done for you.

You should refer to the *RC* circuit in **Figure 6** and to  $V_U$  and  $V_L$  in your answer.

**[3 marks]**

**Stage 1:** Since  $V_c$  is LOW, the output is HIGH.

**Stage 2:** The capacitor now charges through the resistor, making  $V_c$  rise.

**Stage 3:** \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**Stage 4:** \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**Stage 5:** \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**Question 4 continues on the next page**


**Turn over ►**



**0 4 . 2** Figure 7 shows the oscillator circuit after it has been modified by the addition of:

- two diodes  $D_1$  and  $D_2$
- a potential divider that has a total resistance value of  $(R_A + R_B)$ .

**Figure 7**

 

In this particular circuit:

- the time  $t_H$  for the output signal to be HIGH is given by  $t_H = 0.7C(R + R_B)$
- the time  $t_L$  for the output signal to be LOW is given by  $t_L = 0.7C(R + R_A)$ .



The slider of the potential divider is moved towards **X**, as shown in **Figure 7**.

State and explain the effect of this change on:

- the mark-to-space ratio ( $t_H : t_L$ )
- the pulse rate frequency (PRF).

**[4 marks]**

mark-to-space ratio \_\_\_\_\_

---

---

---

---

---

---

PRF \_\_\_\_\_

---

---

---

---

---

---

7

**Turn over for the next question**

**Turn over ►**




0 5

**Figure 8** shows island **A**, a fully developed island off the mainland coast. The island is connected to the mainland by a fibre optic cable lying along the seabed and it also has a satellite link.

Nobody lives on island **B**, but it is due to be developed as a major holiday resort over the next 5 years.

Moveable oil rig **C** is due to explore the four sites marked 'X' for oil and gas over a 9-month period.

**Figure 8**

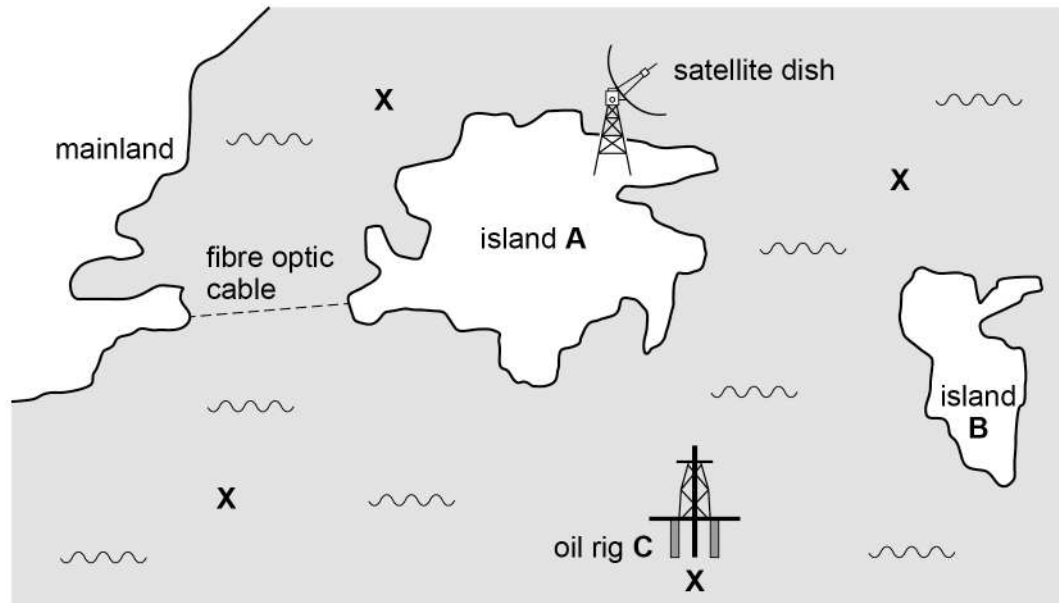

A communications company has been asked to provide solutions for island **B** which will allow the development to begin immediately and then later to support a fully developed holiday resort.

A communications solution is also required for oil rig **C** during the 9-month exploration period.

Describe appropriate solutions involving fibre optic cabling and satellite communication systems for each of the two clients, island **B** and oil rig **C**.

In your answer you should:

- outline the way each communications system operates
- suggest, with reasons, your choice of system for each solution.

**[6 marks]**

---



---



---





**There are no questions printed on this page**

*Do not write  
outside the  
box*

**DO NOT WRITE ON THIS PAGE  
ANSWER IN THE SPACES PROVIDED**











**There are no questions printed on this page**

*Do not write  
outside the  
box*

**DO NOT WRITE ON THIS PAGE  
ANSWER IN THE SPACES PROVIDED**

**Copyright information**

For confidentiality purposes, all acknowledgements of third-party copyright material are published in a separate booklet. This booklet is published after each live examination series and is available for free download from [www.aqa.org.uk](http://www.aqa.org.uk).

Permission to reproduce all copyright material has been applied for. In some cases, efforts to contact copyright-holders may have been unsuccessful and AQA will be happy to rectify any omissions of acknowledgements. If you have any queries please contact the Copyright Team.

Copyright © 2022 AQA and its licensors. All rights reserved.



2 0



2 2 6 A 7 4 0 8 / 3 B E

IB/M/Jun22/7408/3BE